

### HW#3

- 1) Design a Single Cell - 1 bit Carry Propagate (Ripple Carry Adder) full adder.
  - (a) Generate the truth table.
  - (b) Using K-map, determine the logical expression for carry out (C-out) and Sum(s).
  - (c) Based on the logical expression, create the ~~base~~ schematic diagram for full adder.

(a)

A	B	Cin	Sum	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

(b)

A \ B Cin	00	01	11	10
0	0	1	0	1
1	1	0	1	0

Sum

$$\begin{aligned}
 \text{Sum} &= \bar{A}\bar{B}C_{in} + \bar{A}B\bar{C}_{in} + A\bar{B}\bar{C}_{in} + AB C_{in} \\
 &= \bar{A}(\bar{B}C_{in} + B\bar{C}_{in}) + A(\bar{B}\bar{C}_{in} + B C_{in}) \\
 &= \bar{A}(B \oplus C_{in}) + A(B \oplus C_{in}) \\
 &= \bar{A}(B \oplus C_{in}) + A(B \oplus C_{in})
 \end{aligned}$$

$$\text{Sum} = A \oplus B \oplus C_{in}$$


A \ B Cin	00	01	11	00
0	0	0	1	0
1	0	1	1	1

Cout

$$\text{Cout} = ABC + AB\bar{C} + A\bar{B}C + \bar{A}BC$$

$$= AB + (A\bar{B} + \bar{A}B)C$$

$$\text{Cout} = AB + (A \oplus B)C$$

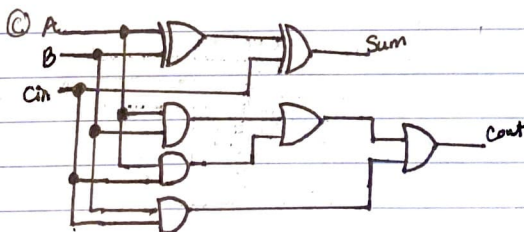

2) Design a 1 bit, 2 to 1 multiplexer (Mux). outputs  $y$  when  $S=0$ ;  $x$  when  $S=1$

(a) Generate the truth table

(b) Using K-map, determine the logical expression for output.

(c) Based on the logical expression, create the schematic diagram for Mux.

a)

S	$I_1$	$I_0$	$y$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

b)

$y$	$\bar{I}_1\bar{I}_0$	$\bar{I}_1I_0$	$I_1\bar{I}_0$	$I_1I_0$
$\bar{S}$	0	1	1	0
$S$	0	0	1	1

$$y = \bar{S}I_0 + SI_1$$

c)

